

Power Design Made Easy!

National Speeds Power Design with a Suite of Online Tools.

WEBENCH® Design Tools
Design, optimize, and build power supply circuits using this FREE online design and prototyping environment.
webench.national.com

Power Reference Designs
National's power reference design library provides a comprehensive library of practical reference designs to speed system design and time-to-market.
www.national.com/refdesigns


News@National
New products and design tools with video tutorial in each issue.
www.national.com/newsletter

Power Designer
Expert tips, tricks, and techniques for powerful designs. Sign up for email alerts when new issues are available.
power.national.com/designer

power.national.com



Power Management IC Wallchart 2007

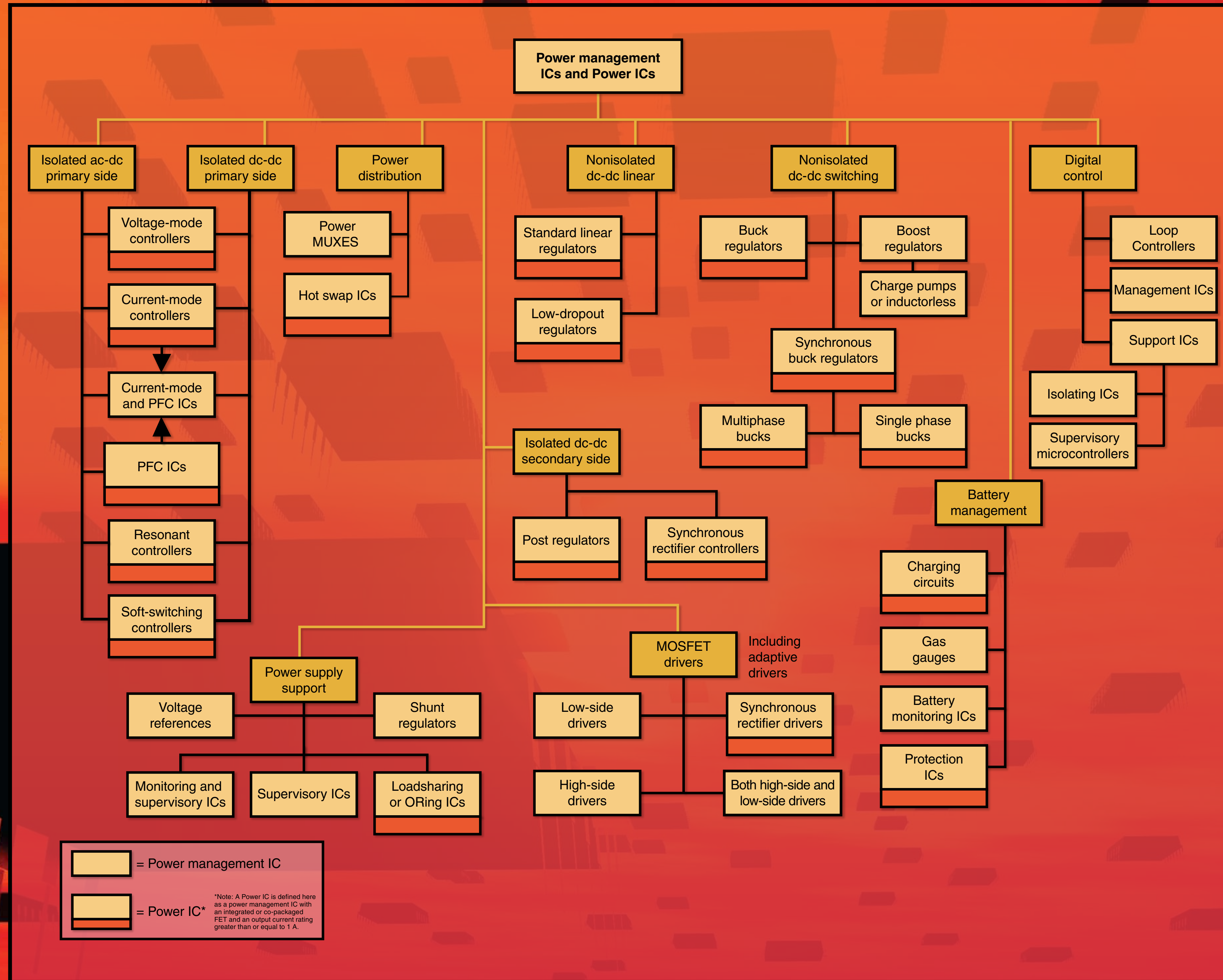

Central Semiconductor Corp. Power Management Discretes

Schottky Rectifiers 1.0 Amp			
• CTLSH1-40	40V, $V_F=0.55V$, $I_R=50\mu A@15V$	SOT-563	
• CTLSH1-40M322	40V, $V_F=0.55V$, $I_R=50\mu A@15V$	TLM322	
• CTLSH1-40M32D	40V, $V_F=0.55V$, $I_R=50\mu A@15V$	TLM32D	
• CMMSH1-20	20V, $V_F=0.45V$, $I_R=500\mu A$	SOD-123F	
• CMMSH1-40	40V, $V_F=0.55V$, $I_R=500\mu A$	SOD-123F	
• CMMSH1-60	60V, $V_F=0.70V$, $I_R=500\mu A$	SOD-123F	
• CMMSH1-100	100V, $V_F=0.85V$, $I_R=500\mu A$	SOD-123F	
• CMMSH1-40L	40V, $V_F=0.45V$, $I_R=500\mu A$	SOD-123F	
• CMPSH1-4	40V, $V_F=0.55V$, $I_R=100\mu A@30V$	SOT-23F	
• CMSH1-20ML	20V, $V_F=0.38V$, $I_R=500\mu A$	SMA	
• CMSH1-40ML	40V, $V_F=0.40V$, $I_R=500\mu A$	SMA	
• CXSH-4	40V, $V_F=0.55V$, $I_R=1,000\mu A$	SOT-89	

Schottky Rectifiers 2.0 Amp			
• CTLSH2-40M32	40V, $V_F=0.50V$, $I_R=200\mu A$	TLM32	
• CMSH2-40L	40V, $V_F=0.40V$, $I_R=500\mu A$	SMB	
• CZSH-4	40V, $V_F=0.60V$, $I_R=1,000\mu A$	SOT-223	


Schottky Rectifiers 3.0 Amp			
• CTLSH3-30M33	30V, $V_F=0.45V$, $I_R=1.0mA$	TLM33	
• CMSH3-20MA	20V, $V_F=0.50V$, $I_R=500\mu A$	SMA	
• CMSH3-40MA	40V, $V_F=0.50V$, $I_R=500\mu A$	SMA	
• CMSH3-60MA	60V, $V_F=0.70V$, $I_R=500\mu A$	SMA	
• CMSH3-100MA	100V, $V_F=0.85V$, $I_R=500\mu A$	SMA	
• CMSH3-20M	20V, $V_F=0.55V$, $I_R=500\mu A$	SMB	
• CMSH3-40M	40V, $V_F=0.55V$, $I_R=500\mu A$	SMB	
• CMSH3-60M	60V, $V_F=0.75V$, $I_R=500\mu A$	SMB	
• CMSH3-100M	100V, $V_F=0.85V$, $I_R=500\mu A$	SMB	
• CMSH3-20L	20V, $V_F=0.38V$, $I_R=500\mu A$	SMC	
• CMSH3-40L	40V, $V_F=0.40V$, $I_R=500\mu A$	SMC	
• CSHD3-40	40V, $V_F=0.65V$, $I_R=100\mu A$	DPAK	
• CSHD3-60	60V, $V_F=0.75V$, $I_R=30\mu A$	DPAK	
• CSHD3-100	100V, $V_F=0.85V$, $I_R=30\mu A$	DPAK	

Schottky Rectifiers 5.0 Amp			
• CTLSH5-40M33	40V, $V_F=0.52V$, $I_R=200\mu A$	TLM33	
• CZSH5-40	40V, $V_F=0.55V$, $I_R=3.0mA$	SOT-223	
• CMSH5-20	20V, $V_F=0.55V$, $I_R=3.0mA$	SMC	
• CMSH5-40	40V, $V_F=0.55V$, $I_R=3.0mA$	SMC	
• CMSH5-60	60V, $V_F=0.75V$, $I_R=3.0mA$	SMC	
• CMSH5-100	100V, $V_F=0.85V$, $I_R=3.0mA$	SMC	
• CSHD5-40	40V, $V_F=0.55V$, $I_R=0.2mA$	DPAK	
• CSHD5-60	60V, $V_F=0.75V$, $I_R=0.2mA$	DPAK	
• CSHD5-100	100V, $V_F=0.85V$, $I_R=0.2mA$	DPAK	
• CSHD5-25L	25V, $V_F=0.47V$, $I_R=500\mu A$	DPAK	

www.centralsemi.com
145 Adams Avenue • Hauppauge • New York • 11788 • USA • Tel: (631) 435-1110 • Fax: (631) 435-1824



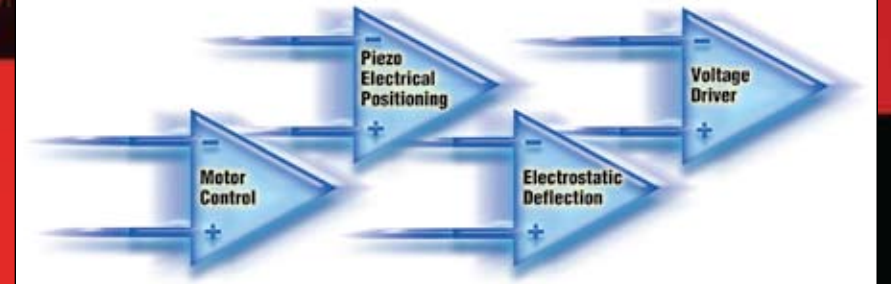Reliable Choices in Power Amplifier Solutions
Apex delivers high current and high voltage amplifiers for precision control applications



Precision ICs ... Military Grade Hybrids ... Power Open Frame Modules

Apex has more than 120 models of IC and hybrid power amplifiers. When you are looking for output current greater than 1A, or total supply voltages above 100V, then Apex is the reliable choice. Through a combination of exceptional performance, manufacturing integrity and long product life cycles, Apex helps customers manage component obsolescence.




Visit us online today at www.apexmicrotech.com/POWER or call 1-800-862-1020



Power products and support for your design challenges!

power.ti.com

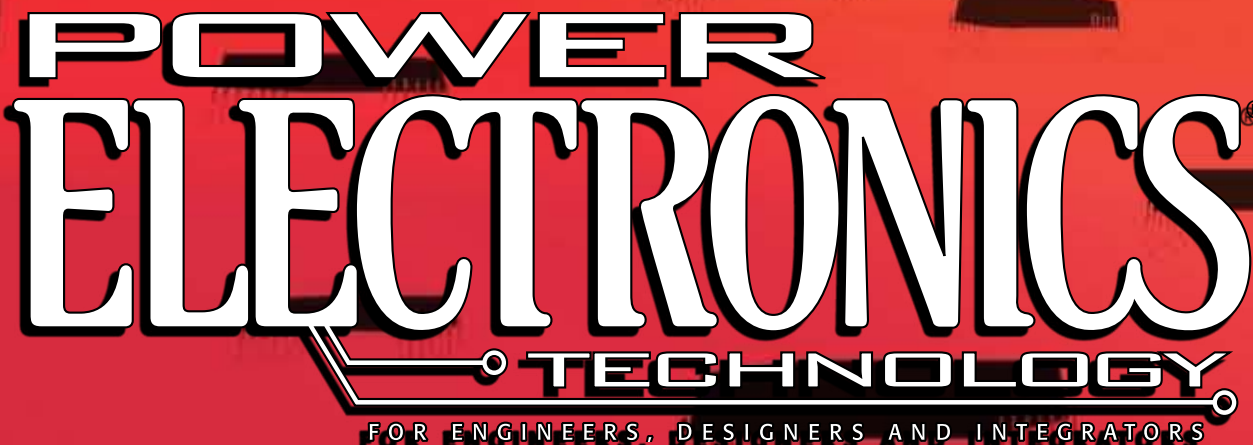

Technology for Innovators™

TEXAS INSTRUMENTS